
Amp Documentation

The Amplifier project contains 5 modular parts.

- 15volt 7+amp power supply
- 5volt 1amp power supply
- Audio amplifier with 2 channels, 35watt per channel.
- Stereo Audio integrator (to smooth out dot-bar display)
- 2x dot bar display (one for each channel)

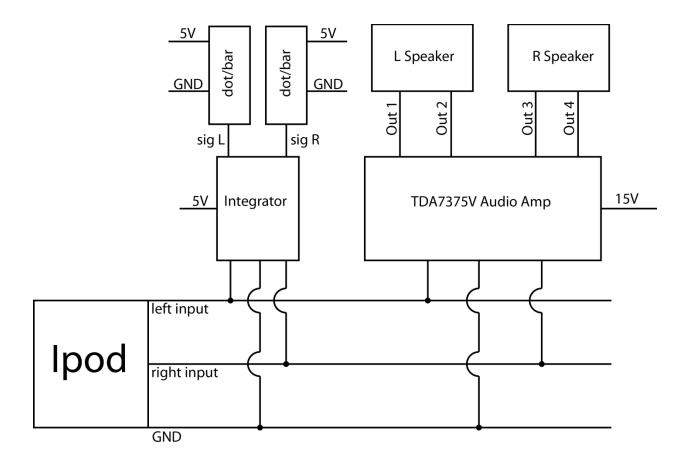In this project an audio signal from an ipod or other low-voltage audio device, is measured by a volume meter and amplified by a TDA7375V.



Electrical Characteristics and Parameters

- Ipod
 - Voltages of up to ±1.5 volts relative to GND
- Audio Amp
 - o Voltage range 8V to 18V
 - Max output power: 35 watts per channel
 - Voltage gain 26 db ≈ 19.95
- Integrator
 - Max supply and input voltages of 5V
- Dot-Bar display
 - Able to map from 0V to (Supply Voltage -1.5V)
 - R1 (initially set to 3.3k) changes mapping range
 - Check the range by measuring voltage on pin 6
 - When R1 = 220 Ω ; Ref_{high} ≈ 1.5volts
 - o Pushbutton
 - down = bar mode
 - up = dot mode
 - a wire can be used instead of a button for always bar mode
 - Clip plus and Clip minus can be connected to the audio amp

Notes:

GND means Ground and each ground for every circuit should be connected together

- Ipod
 - Voltages can be measured using the oscilloscope. This is good for eyeballing the voltage it produces when at certain volume levels
- Audio Amp
 - C = clip+
 - o + = +15V
 - S = GND
 - o G = GND
 - 1/3 means audio input left/right or channel1/channel2
 - Output 1 & 2 are connected to input 1
 - Output 3 & 4 are connected to input 3
 - The device will be in stand-by (not playing music) when the voltage on the stand-by pin is less than 5V
 - The ST-BY pin can withstand 15V given a strong resistor 10k+
- Integrator
 - Is two channel (it can run two dot bar displays)
 - Potentiometers can be replaced with wire because they only divide the voltage from the ipod

- The integrator acts as a 0 voltage drop diode, therefor, polarized caps can be kept from reverse polarization
- o Both [GND and 5V] terminals are in parallel for convenience